




Semiconductor Electronics: Materials, Devices and Simple Circuits

Q.No.1:


The I-V characteristic of an LED is:

JEE 2013


A.

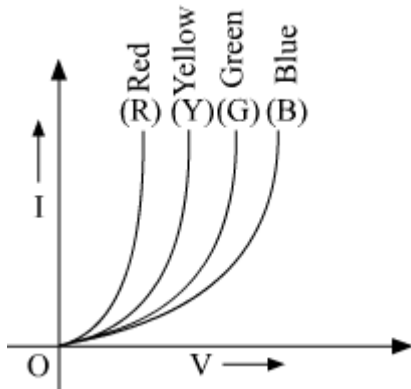


B.

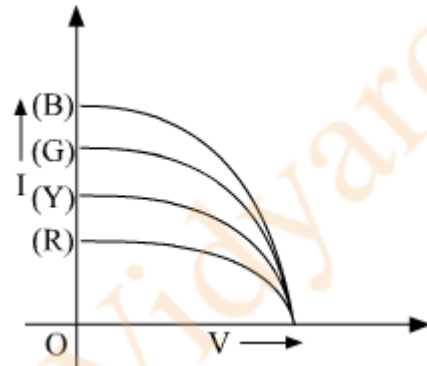

C.

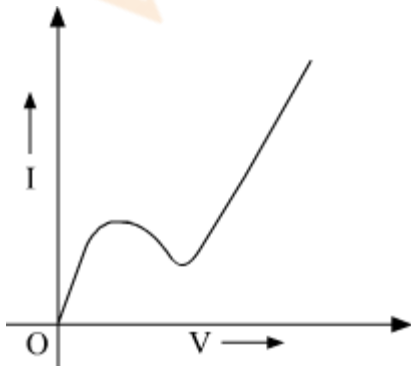

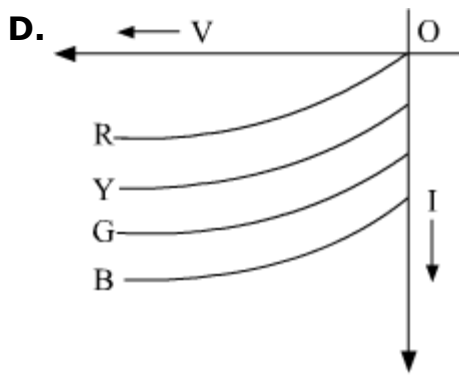

Q.No.2: The forward-biased diode connection is


- A.**
- B.**
- C.**
- D.**

Q.No.3: For a common emitter configuration, if α and β have their usual meanings, the incorrect relationship between α and β

JEE 2016


- A.** $\alpha = \frac{\beta}{1-\beta}$
- B.** $\alpha = \frac{\beta}{1+\beta}$
- C.** $\alpha = \frac{\beta^2}{1+\beta^2+2\beta}$
- D.** $\frac{1}{\alpha} = \frac{1}{\beta} + 1$

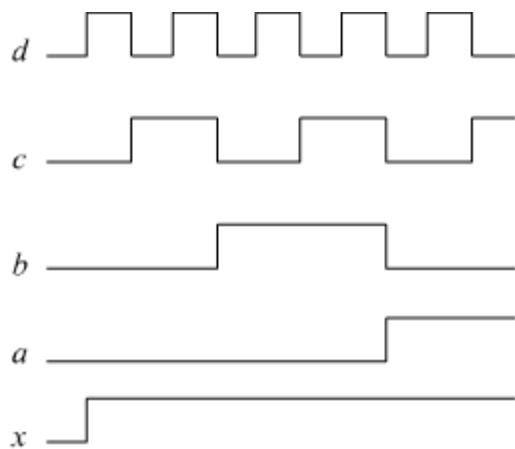Q.No.4: If a, b, c, d are inputs to a gate and x is its output, then, as per the following time graph, the gate is:



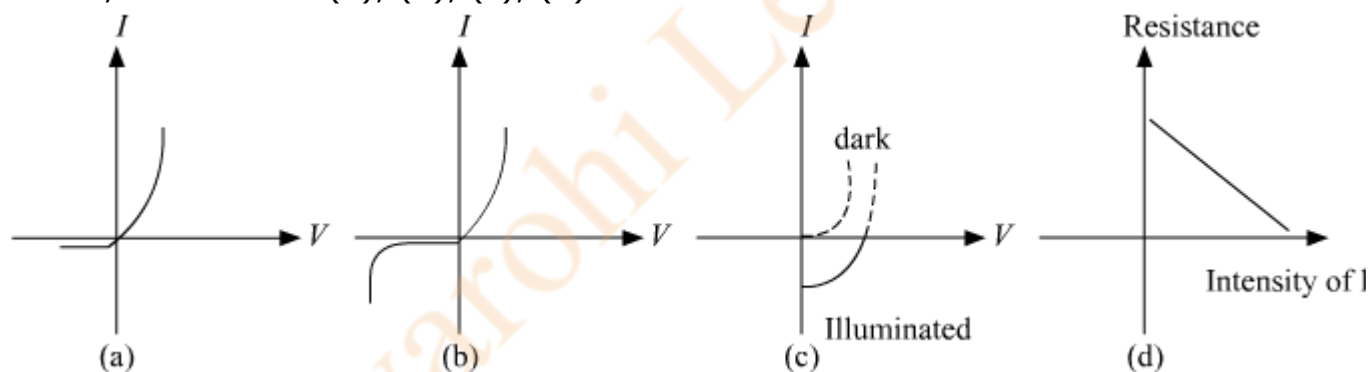- A. AND
- B. OR
- C. NAND
- D. NOT

Q.No.5: Identify the semiconductor devices whose characteristics are given below, in the order (a), (b), (c), (d):



- A. Zener diode, Simple diode, Light dependent resistance, Solar cell
- B. Solar cell, Light dependent resistance, Zener diode, Simple diode
- C. Zener diode, solar cell, Simple diode, Light dependent resistance
- D. Simple diode, Zener diode, Solar cell, Light dependent resistance


Q.No.6: The temperature dependence of resistances of Cu and undoped Si in the temperature range 300-400K, is best described by:

- A. Linear increase for Cu, exponential increase for Si
- B. Linear increase for Cu, exponential decrease for Si
- C. Linear decrease for Cu, linear decrease for Si
- D. Linear increase for Cu, linear increase for Si

Q.No.7: In a common emitter amplifier circuit using an n-p-n transistor, the phase difference between the input and the output voltages will be: **JEE 2017**

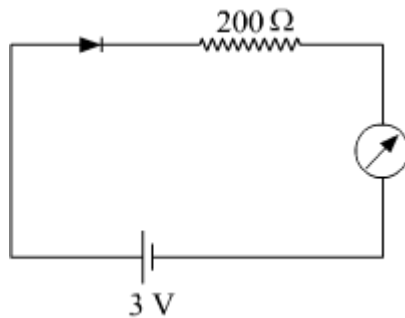- A. 180°
- B. 45°
- C. 90°
- D. 135°

Q.No.8: The reading of the ammeter for a silicon diode in the given circuit is : **JEE 2018**




- A. 11.5 mA
- B. 13.5 mA
- C. 0
- D. 15 mA

Q.No.9: Mobility of electrons in a semiconductor is defined as the ratio of their drift velocity to the applied electric field. If, for an n-type semiconductor, the density of electrons is 10^{19} m^{-3} and their mobility is $1.6 \text{ m}^2/(\text{V}\cdot\text{s})$ then the resistivity of the semiconductor (since it is an n-type semiconductor contribution of holes is ignored) is close to: **JEE 2019**

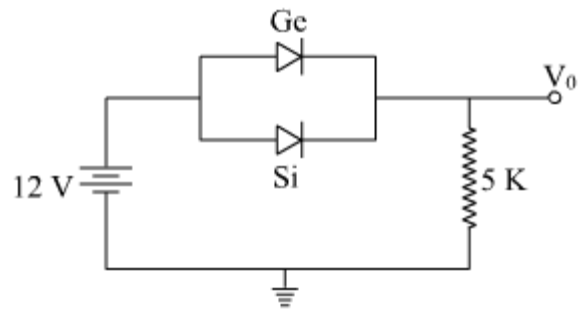- A. $2 \Omega\text{m}$
- B. $4 \Omega\text{m}$
- C. $0.4 \Omega\text{m}$
- D. $0.2 \Omega\text{m}$

Q.No.10: Ge and Si diodes start conducting at 0.3 V and 0.7 V respectively. In the following figure if Ge diode connection are reversed, the value of V_0 changes by: (assume that the Ge diode has large breakdown voltage)



- A. 0.8 V
- B. 0.6 V
- C. 0.2 V
- D. 0.4 V

Vidyarohi Learning