



Current Electricity

Q.No.1:

The supply voltage to a room is 120 V. The resistance of the lead wires is 6Ω . A 60 W bulb is already switched on. What is the decrease of voltage across the bulb, when a 240 W heater is switched on in parallel to the bulb?


JEE 2013

- A. Zero Volt
- B. 2.9 Volt
- C. 13.3 Volt
- D. 10.04 Volt

Q.No.2: In a large building, there are 15 bulbs of 40 W, 5 bulbs of 100 W, 5 fans of 80 W and 1 heater of 1 kW. The voltage of the electric mains is 220 V. The minimum capacity of the main fuse of the building will be

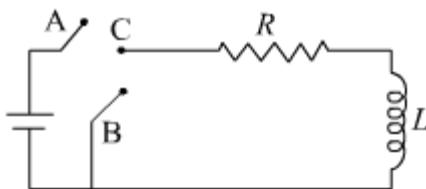- A. 12 A
- B. 14 A
- C. 8 A
- D. 10 A

Q.No.3: In the circuit shown here, point C is kept connected to point A till the current flowing through the circuit becomes constant. Afterwards, suddenly, point C is disconnected from point A and connected to point B at time $t = 0$. Ratio of the voltage across resistance and the inductor at $t = L/R$ will be equal to



- A. -1
- B. $\frac{1-e}{e}$

C. $\frac{e}{1-e}$

D. 1

Q.No.4: When 5 V potential difference is applied across a wire of length 0.1 m, the drift speed of electrons is $2.5 \times 10^{-4} \text{ ms}^{-1}$. If the electron density in the wire is $8 \times 10^{28} \text{ m}^{-3}$, the resistivity of the material is close to: **JEE 2015**

A. $1.6 \times 10^{-8} \Omega\text{m}$


B. $1.6 \times 10^{-7} \Omega\text{m}$

C. $1.6 \times 10^{-6} \Omega\text{m}$

D. $1.6 \times 10^{-5} \Omega\text{m}$

Q.No.5: In the circuit shown, the current in the 1Ω resistor is :

JEE 2015

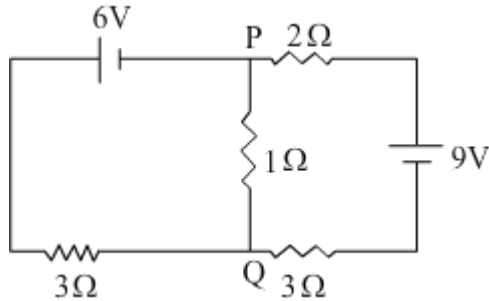

A. 1.3 A, from P to Q

B. 0 A

C. 0.13 A, from Q to P

D. 0.13 A, from P to Q

Q.No.6: A galvanometer having a coil resistance of 100Ω gives a full scale deflection, when a current of 1 mA is passed through it. The value of the resistance, which can convert this galvanometer into ammeter giving a full scale deflection for a current of 10 A, is :

JEE 2016

A. 2Ω

B. 0.1Ω

C. 3Ω

D. 0.01Ω

Q.No.7: In the above circuit the current in each resistance is:


JEE 2017

A. 0 A

- B. 1 A
- C. 0.25 A
- D. 0.5 A

Q.No.8: In the given circuit diagram when the current reaches a steady state in the circuit, the charge on the capacitor of capacitance C will be:

JEE 2017

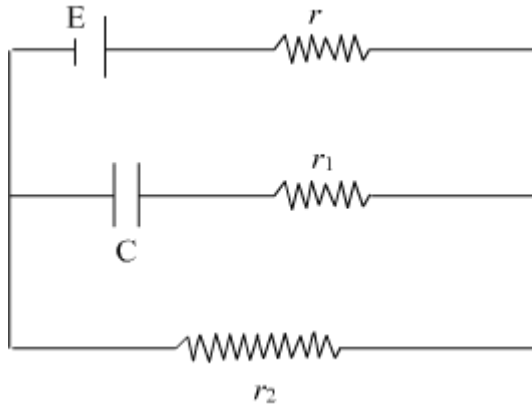

- A. $CE \frac{r_1}{(r_1 + r)}$
- B. CE
- C. $CE \frac{r_1}{(r_2 + r)}$
- D. $CE \frac{r_2}{(r + r_2)}$

Q.No.9: Which of the following statements is false?

JEE 2017

- A. Krichhoff's second law represents energy conservation.
- B. Wheatstone bridge is the most sensitive when all the four resistance are of the same order of magnitude.
- C. In a balanced wheatstone bridge if the cell and the galvanometer are exchanged, the null point is disturbed.
- D. A rheostat can be used as a potential divider.

Q.No.10: Two batteries with e.m.f. 12 V and 13 V are connected in parallel across a load resistor of $10\ \Omega$. The internal resistances of the two batteries are $1\ \Omega$ and $2\ \Omega$ respectively. The voltage across the load lies between : **JEE 2018**

- A.** 11.4 V and 11.5 V
- B.** 11.7 V and 11.8 V
- C.** 11.6 V and 11.7 V
- D.** 11.5 V and 11.6 V

Vidyarohi Learning